

1315**Code : 15EE61T***Register
Number*

--	--	--	--	--	--	--	--	--	--

VI Semester Diploma Examination, Nov./Dec.-2018
INDUSTRIAL DRIVES & CONTROL

Time : 3 Hours |**| Max. Marks : 100**

- Note :** (i) Answer any **six** questions from Part – A. (Each question carries **5** marks)
(ii) Answer any **seven** questions from Part – B. (Each question carries **10** marks)

PART – A**BETA CONSOLE!**

1. Draw the block diagram of an Electric drive. 5
2. Select suitable drive for the following and justify the same : 5
 - (a) Cane cutters
 - (b) Cane crushing mills
3. Select suitable drive for large centrifugal pump and justify the same. 5
4. Define open loop and closed loop systems. 5
5. Draw the symbols for the following : 5
 - (a) ON push button
 - (b) OFF push button
 - (c) Coil
 - (d) Limit switch
 - (e) Float switch
6. Draw 2-wire and 3-wire control circuit for controlling an induction motor. 5
7. Develop control circuit for controlling an induction motor from one location. 5
8. Develop control circuit for jogging control of an induction motor. 5
9. List the advantages of Electric traction. 5

PART – B

10. Explain multiquadrant operation of electric drive. 10
11. Draw the process flow diagram of sugar mill and explain various processes. 10
12. Draw the process flow diagram of cement mill for dry process and explain. 10
13. Explain the operation of thermostat switch with a diagram. 10
14. Develop control circuit for the following :
- (a) Forward and reverse control of an Induction motor. 5
 - (b) Fully automatic star-delta starter. 5
15. Draw and explain the basic structure of computer controlled system. 10
16. (a) Draw the block diagram of computer integrated manufacturing system. 5
- (b) Draw the block diagram of clinker burning control in a cement plant. 5
17. Describe chopper controlled drive for DC motor with composite braking for DC fraction system. 10
18. Draw and name the parts of the following speed time curves :
- (a) City service 3
 - (b) Sub-urban service 3
 - (c) Main line service 4
19. (a) List the advantages of electric braking. 5
- (b) Explain with diagram current collection through single arm pantograph collector. 5